#### /electronics

#### Code and Space ARC 593 | DMS 606

Fall 2016


Instructor: Mark Shepard TA: Leonardo Aranda

### electricity

- a fundamental form of energy observable in positive and negative forms that occurs naturally (as in lightning) or is produced (as with a generator) and that is expressed in terms of the movement and interaction of electrons.
- an electron is a subatomic particle with a negative elementary electric charge.
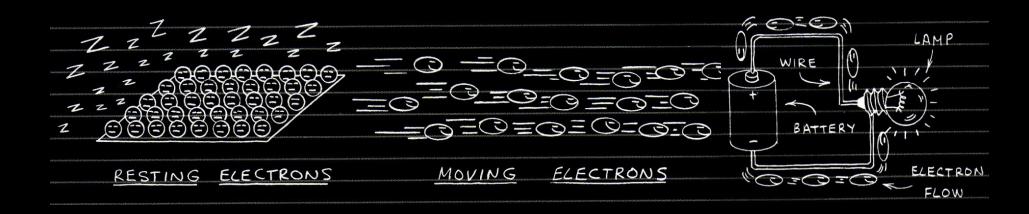
### electricity

 electrons are resting until a closed loop is formed between positive and negative: when the loop is closed, electrons start moving.





#### transduction

- conversion of one energy type to another energy type
  - electricity > light
  - electricity > heat
  - electricity > movement
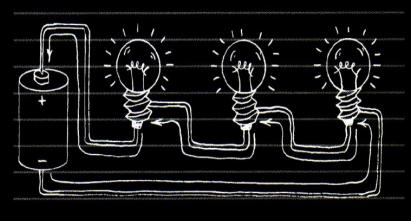
#### circuits

- are devices that work by controlling the flow of electrons through electrical components
- are a closed path formed by interaction of electrical components through which the electric current can flow.



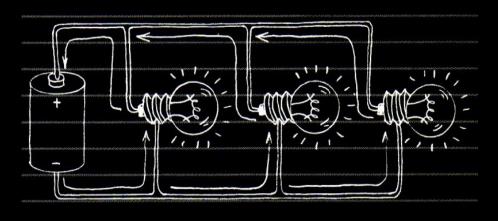


series

parallel
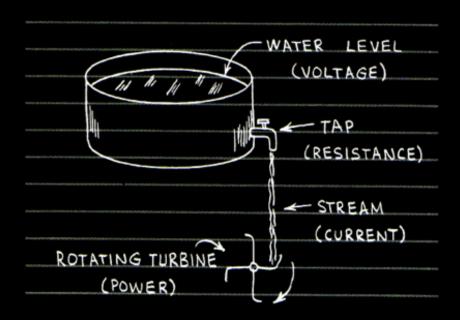
### terminology


- voltage (V), unit: Volts (V) potential difference in the circuit
- resistance (R), unit: Ohm  $(\Omega)$  a measure of the degree to which an object resists an electrical current through it
- current (I), unit: Ampere (A) quantity of electrons passing a given point
- power (P), unit: Watt (W) work done by electrical current



#### resistors

- Resistors resist, but do not totally block, the flow of electricity.
- They are used to control the flow of current.
  Current can move either way through a resistor, so it doesn't matter which way they're connected in a circuit.
- Resistors are measured by their resistance in ohms  $(\Omega)$ , often seen in kilohms  $(k\Omega)$ .

#### resistors

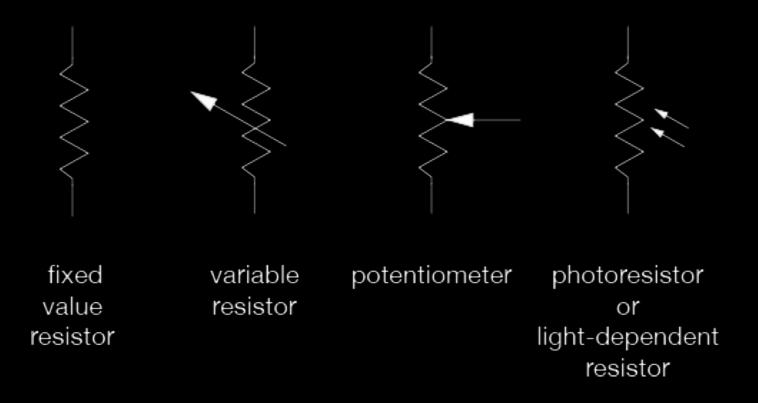


> Resistor Color Code Calculator

### capacitors

- Capacitors store up electricity while current is flowing into them, then release the energy when the incoming current is removed.
- Capacitors are measured by their capacitance in farads (F), most commonly seen in microfarads (µF).
- Sometimes they are polarized, meaning current can only flow through them in a specific direction, and sometimes they are not.

## capacitors

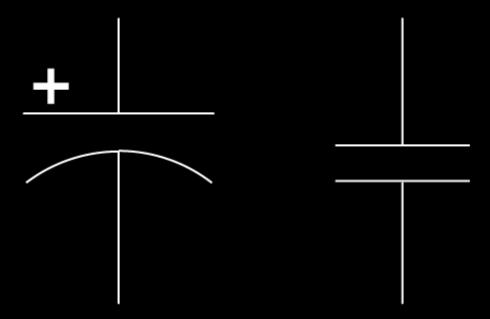


polarized capacitor

non-polarized capacitor

#### diodes


- diodes permit the flow of electricity in one direction, and block it in the other direction.
- because of this, they can only be placed in a circuit in one direction.
- Light-Emitting Diodes (LED's) are special types of diodes which emit light when current flows through them.

### diodes

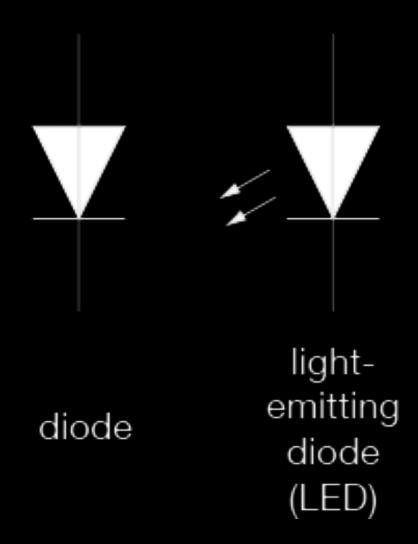

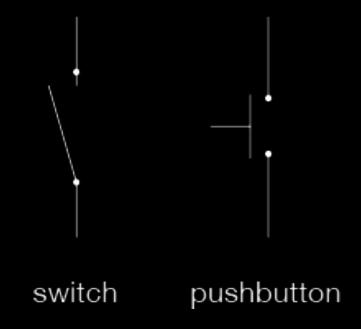
### switches

 switches and pushbuttons control the flow of current through a junction in a circuit



### transistors and relays

are electrical switching devices

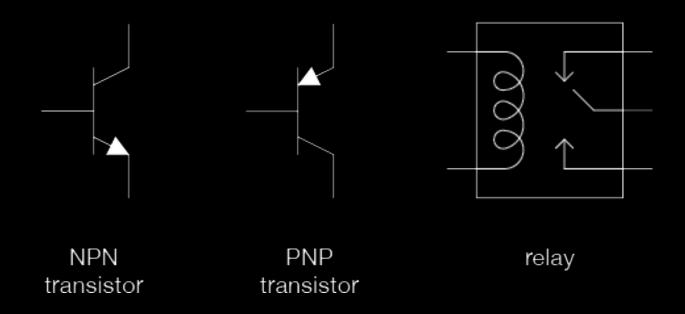

#### ohm's law

 for a given resistance, voltage across the two points is directly proportional to the current between them

V = I \* R

# using a multimeter



## soldering

